

CS2100

TUTORIAL #6

BOOLEAN ALGEBRA, LOGIC GATES & SIMPLIFICATION

(PREPARED BY: AARON TAN)

Q1. Consensus theorem

$$x \cdot y + x' \cdot z + y \cdot z = x \cdot y + x' \cdot z$$

		y	
x	0	1	1
	0	0	1
		z	

$$x \cdot y + x' \cdot z + y \cdot z$$

$$= x \cdot y + x' \cdot z + 1 \cdot y \cdot z$$

$$= x \cdot y + x' \cdot z + (x + x') \cdot y \cdot z$$

$$= x \cdot y + x' \cdot z + x \cdot y \cdot z + x' \cdot y \cdot z$$

$$= x \cdot y + x \cdot y \cdot z + x' \cdot z + x' \cdot y \cdot z$$

$$= (x \cdot y + x \cdot y \cdot z) + (x' \cdot z + x' \cdot y \cdot z)$$

$$= x \cdot y + x' \cdot z$$

[identity law]

[complement law]

[distributive law]

[commutative law]

[associative law]

[absorption theorem 1]

$$\text{Q2(a)} \quad F(x,y,z) = (x+y \cdot z') \cdot (y' + y) + x' \cdot (y \cdot z' + y)$$

$$= (x+y \cdot z') \cdot 1 + x' \cdot (y \cdot z' + y)$$

(by the complement law)

$$= (x+y \cdot z') + x' \cdot (y \cdot z' + y)$$

(by the identity law)

$$= x + y \cdot z' + x' \cdot y$$

(by absorption theorem 1)

$$= x + x' \cdot y + y \cdot z'$$

(by the commutative law)

$$= x + y + y \cdot z'$$

(by absorption theorem 2)

$$= x + y$$

(by absorption theorem 1)

Q2(b)

$$5 = (0101)_2; 9 = (1001)_2; 13 = (1101)_2$$

$$G(p,q,r,s) = \Pi M(5, 9, 13)$$

$$= (p+q'+r+s') \cdot (p'+q+r+s') \cdot (p'+q'+r+s') \quad (\text{by definition of maxterms})$$

$$= ((p \cdot p') + (q'+r+s')) \cdot (p'+q+r+s') \quad (\text{by the distributive law})$$

$$(p+(q'+r+s')) \cdot (p'+(q'+r+s')) \\ = (p \cdot p') + (q'+r+s')$$

Distributive law:

$$A + (B \cdot C) = (A+B) \cdot (A+C)$$

$$\text{or } (B \cdot C) + A = (B+A) \cdot (C+A)$$

Q2(b)

$$5 = (0101)_2; 9 = (1001)_2; 13 = (1101)_2$$

$$G(p,q,r,s) = \Pi M(5, 9, 13)$$

$$= (p+q'+r+s') \cdot (p'+q+r+s') \cdot (p'+q'+r+s') \quad (\text{by definition of maxterms})$$

$$= ((p \cdot p') + (q'+r+s')) \cdot (p'+q+r+s') \quad (\text{by the distributive law})$$

$$= (0 + (q'+r+s')) \cdot (p'+q+r+s') \quad (\text{by the complement law})$$

$$= (q'+r+s') \cdot (p'+q+r+s') \quad (\text{by the identity law})$$

$$= (q' \cdot (p'+q)) + (r+s') \quad (\text{by the distributive law})$$

$$= p' \cdot q' + r + s' \quad (\text{by absorption 2})$$


Absorption theorem 2:

$$A \cdot (A' + B) = A \cdot B$$

$$q' \cdot (p' + q) = q' \cdot (q + p') = q' \cdot p' = p' \cdot q'$$

Q3.

(a)

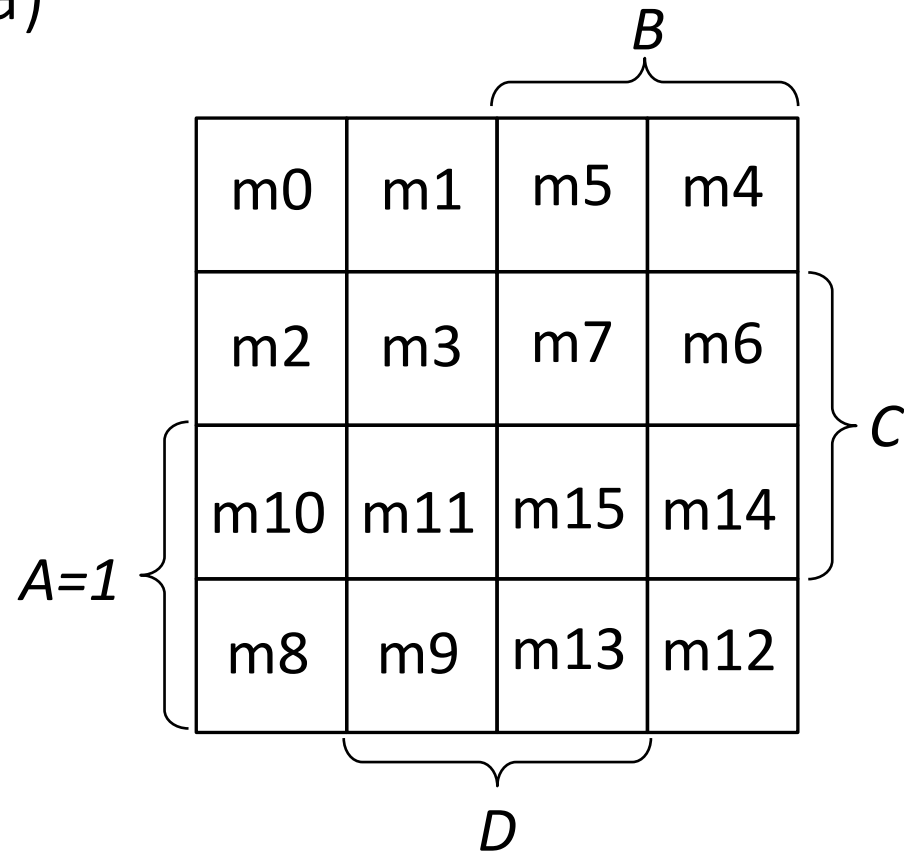

$$m_1: 0001 = A' \cdot B' \cdot C' \cdot D$$

Q3.

(b) $T(A,B,C,D) = \Pi M(3,7,8,10,12,13) \cdot X(6,11,14,15).$
 $T(A,B,C,D) = \Sigma m(0,1,2,4,5,9) + X(6,11,14,15).$

(a)

				B	
A	m0	m1	m5	m4	C
	m2	m3	m7	m6	
	m10	m11	m15	m14	
	m8	m9	m13	m12	
				D	

(c)

				B	
A	1	1	1	1	C
	1	0	0	X	
	0	X	X	X	
	0	1	0	0	
				D	

Q3.

(d) How many Pls: 4

$A'.D', A'.C', B'.C'.D, A.B'.D$

(e) How many EPls: 2

$A'.D', A'.C'$

		B			
		1	1	1	1
		1	0	0	X
		0	X	X	X
		0	1	0	0
					D
A					
					C

Q3. (f) Simplified SOP: $T(A,B,C,D) = A'.C' + A'.D' + B'.C'.D$

$$T(A,B,C,D) = A'.C' + A'.D' + A.B'.D$$

A 4x4 Karnaugh map for the function T(A,B,C,D). The map is organized with variables A and B as row headers and C and D as column headers. The cells contain values 1, 0, or X (don't care). The top row (A=0) is highlighted in yellow. The second row (A=1) has its second column (B=0) highlighted in blue. The third row (A=0) has its second column (B=0) highlighted in blue. The bottom row (A=1) has its second column (B=0) highlighted in blue. Brackets indicate the groupings for the simplified SOP terms: A'.C' (top row, columns 1 and 2), A'.D' (top row, columns 3 and 4), and A.B'.D (rows 2 and 3, column 2).


	B			
	0	1	0	1
A	1	1	1	1
	1	0	0	X
	0	X	X	X
	0	1	0	0
	D		C	

Q3. (g) Simplified POS: $T(A,B,C,D) = (A'+B').(C'+D').(A'+D)$


	B			
	1	1	1	1
	1	0	0	X
A	0	X	X	X
	0	1	0	0
	D			
	C			

Q3. (h) $T(A,B,C,D) = A'.C' + A'.D' + B'.C'.D$

2-level AND-OR circuit:

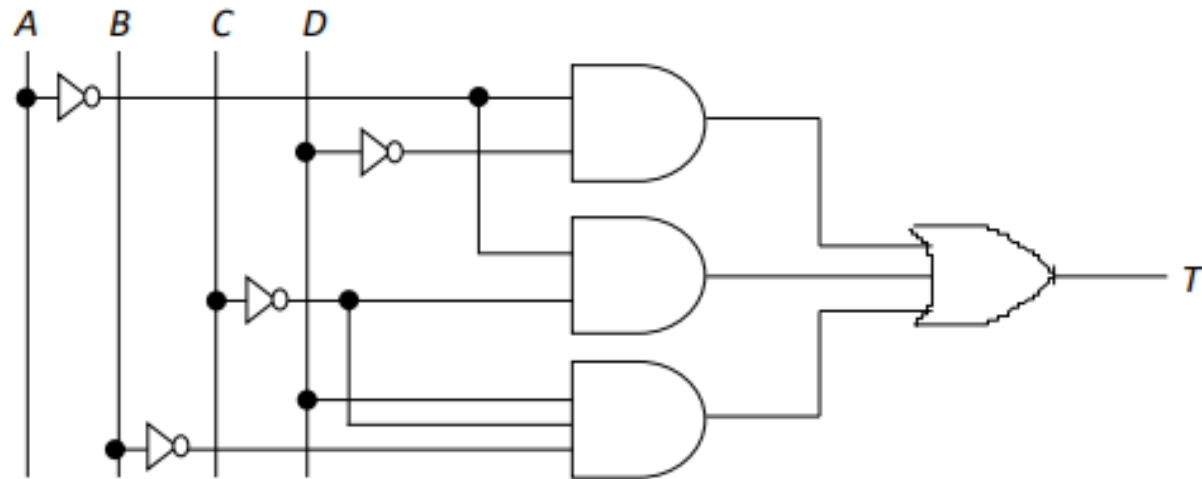

2-level NAND circuit:

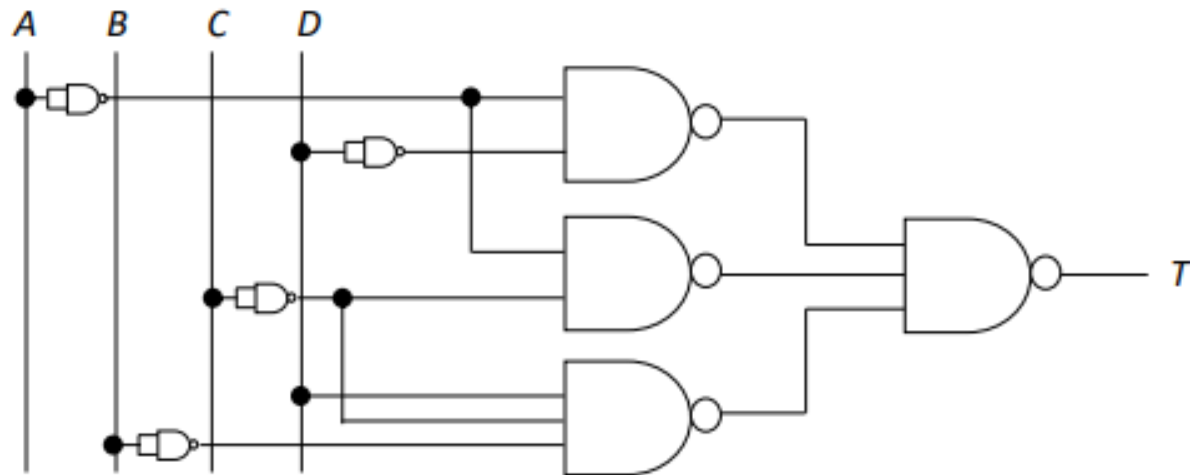


Q4. For output X,

K	L	M	N	X	Y	Z
0	0	0	0	d	d	d
0	0	0	1	0	1	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	1	1	1
0	1	1	0	0	1	1
0	1	1	1	0	1	1

K	L	M	N	X	Y	Z
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	1	0
1	0	1	1	0	1	0
1	1	0	0	0	0	0
1	1	0	1	0	0	0
1	1	1	0	0	0	0
1	1	1	1	1	1	0

(b) **X**

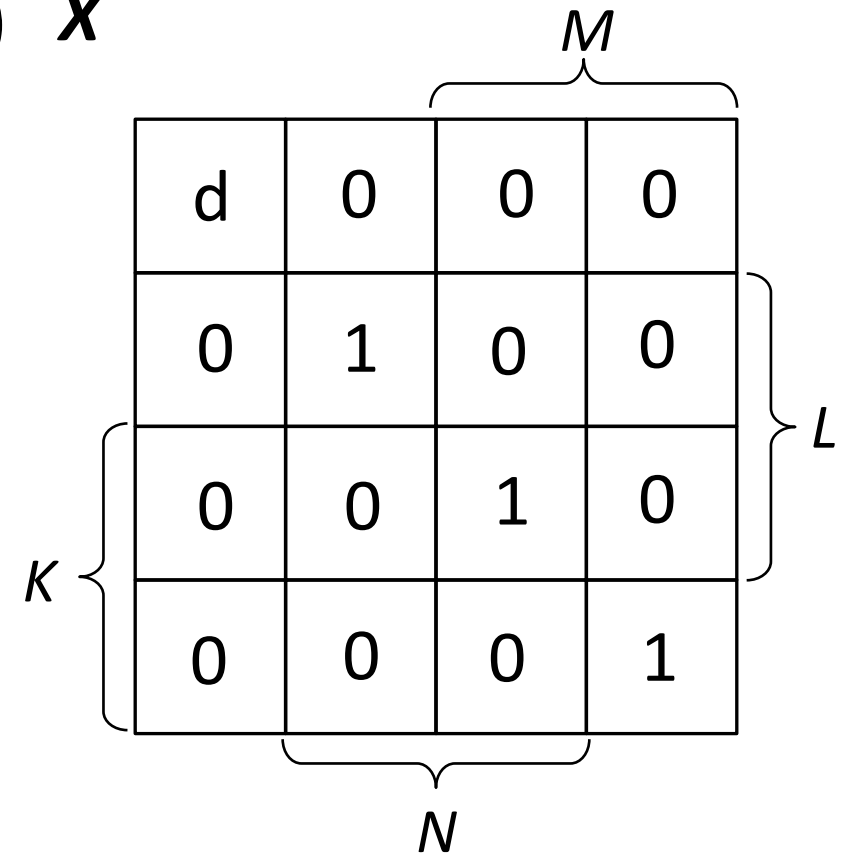

$$(c) X = K' \cdot L \cdot M' \cdot N + K \cdot L' \cdot M \cdot N' + K \cdot L \cdot M \cdot N$$


$$(d) KLMN = 0000 \rightarrow X = 0$$

Q4. (b)(c)(d)

K	L	M	N	X	Y	Z
0	0	0	0	d	d	d
0	0	0	1	0	1	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	1	1	1
0	1	1	0	0	1	1
0	1	1	1	0	1	1

K	L	M	N	X	Y	Z
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	1	0
1	0	1	1	0	1	0
1	1	0	0	0	0	0
1	1	0	1	0	0	0
1	1	1	0	0	0	0
1	1	1	1	1	1	0

(b) Y

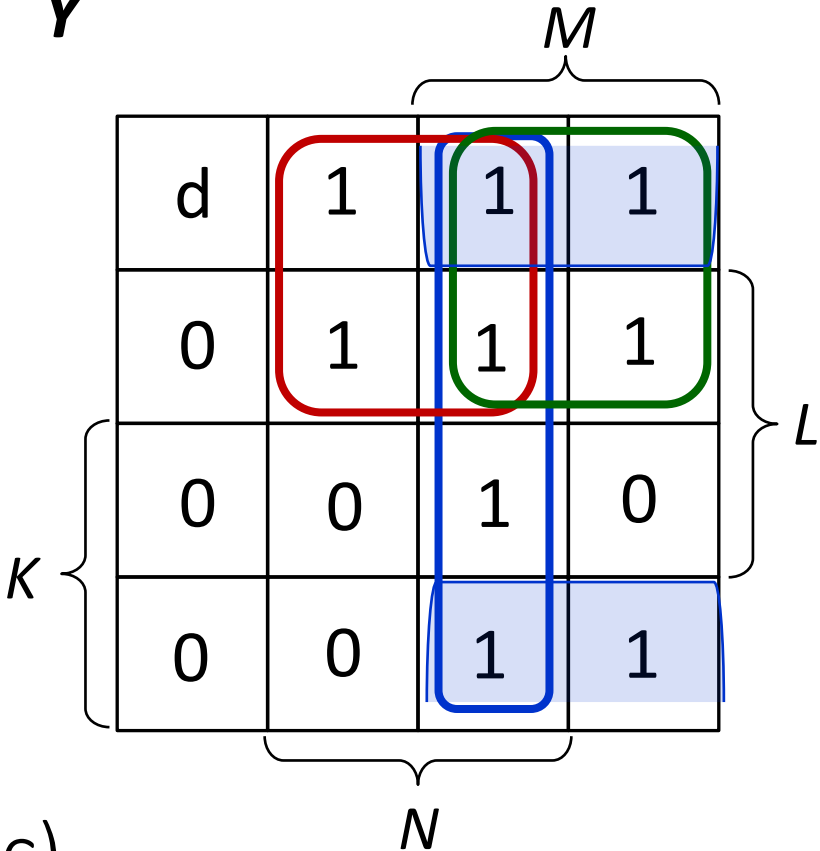

(c)

$$Y = M \cdot N + K' \cdot N + K' \cdot M + L' \cdot M$$

(d)


$$KLMN = 0000 \rightarrow Y = 0$$

Q4. (b)(c)(d)

K	L	M	N	X	Y	Z
0	0	0	0	d	d	d
0	0	0	1	0	1	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	1	1	1
0	1	1	0	0	1	1
0	1	1	1	0	1	1

K	L	M	N	X	Y	Z
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	1	0
1	0	1	1	0	1	0
1	1	0	0	0	0	0
1	1	0	1	0	0	0
1	1	1	0	0	0	0
1	1	1	1	1	1	0

(b) **Z**

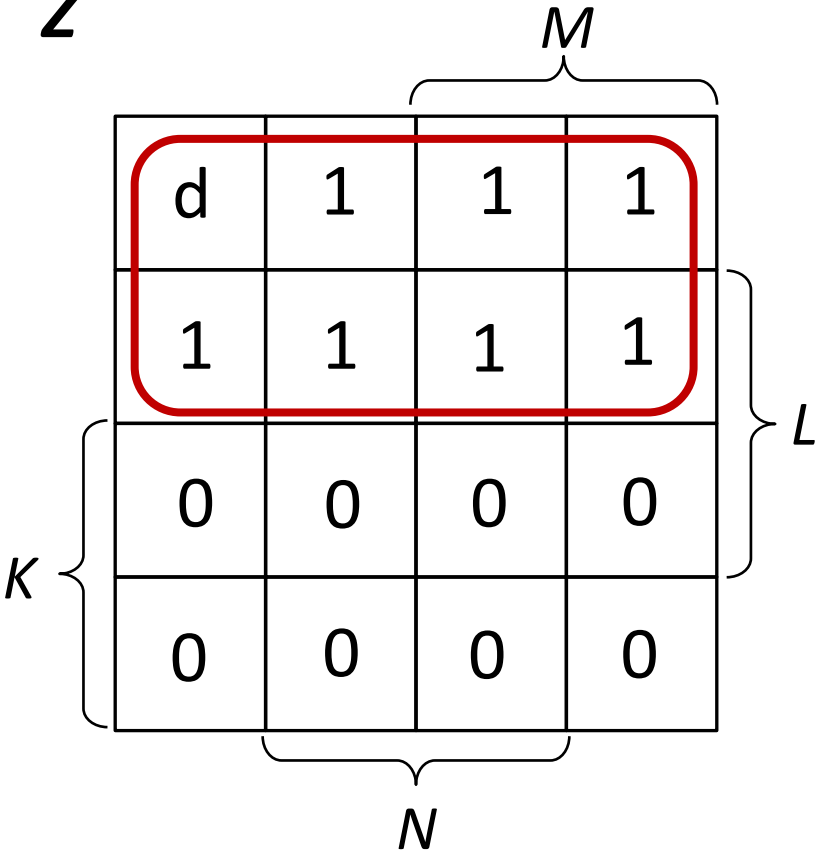

(c) $Z = K'$


(d) $KL MN = 0000 \rightarrow Z = 1$

END OF FILE

All the best for Mid-terms


Bubble Pushing for Converting between Complete Sets of Logic

Notation: Use a bubble to represent an inverter/NOT gate

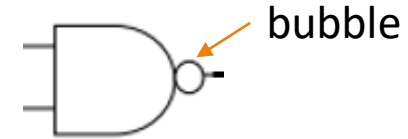

Rule 1: Can create a pair of bubbles at any input/output of a gate.

Reason: Involution Theorem $(A')' \equiv A$

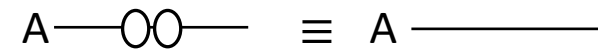

Rule 2: Can push a bubble through a gate by changing the gate from AND to OR and OR to AND

Reason: De Morgan's Theorem $A'B' \equiv (A + B)'$ and $A' + B' \equiv (AB)'$

