

## CS2100 Assignment 3 Answer Book

<b>Name:</b>	Neo Haowei
<b>Student ID:</b>	A0264683U
<b>Tutorial Group Number:</b>	41

Save this file as AxxxxxxxY.pdf and submit on Canvas. You do NOT need to create a zip file.

You will forfeit up to 3 marks if you do not fill your particulars above, or do not follow the submission instructions.

**Submission information:** \_\_\_\_\_ / 3

### Question 1. (6 MARKS)

- (a) (2 marks)  $F(A,B,C,D) = \Sigma m(6, 15)$
- (b) (2 marks)  $G(A,B,C,D) = \Sigma m(8, 10, 12)$
- (c) (2 marks)  $H(D,C,B,A) = \Sigma m(10, 11, 15)$

**Q1 Total:** \_\_\_\_\_ / 6

### Question 2. (6 MARKS)

- (a) (2 marks)  $X(A,B,C) = \Pi M(0, 3, 6, 7)$
- (b) (2 marks)  $Y(A,B,C,D) = \Pi M(0, 1, 2, 3, 6, 7, 8, 10, 11, 13, 14, 15)$
- (c) (2 marks)  $Z(C,B,A) = \Pi M(1, 2, 4, 6)$

**Q2 Total:** \_\_\_\_\_ / 6

### Question 3. (7 MARKS)

- (a) (3 marks)

$$F = A' + (B' \cdot C')$$


$$G = (A' \cdot B) + (B \cdot C') + (A \cdot B' \cdot C)$$

$$H = C$$

- (b) (2 marks)

“The circuit converts a 3-bit sign-and-magnitude number to 3-bit excess 4 code.”

- (c) (2 marks)

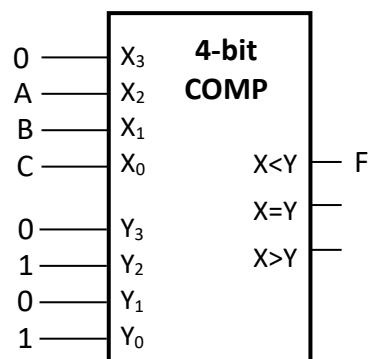


**Q3 Total:** \_\_\_\_\_ / 7


**Question 4. (7 MARKS)**

(a) (2 marks)  $F(A,B,C,D) = (A \cdot C') + (A \cdot B \cdot D') + (B \cdot C' \cdot D')$

(b) (2 marks)

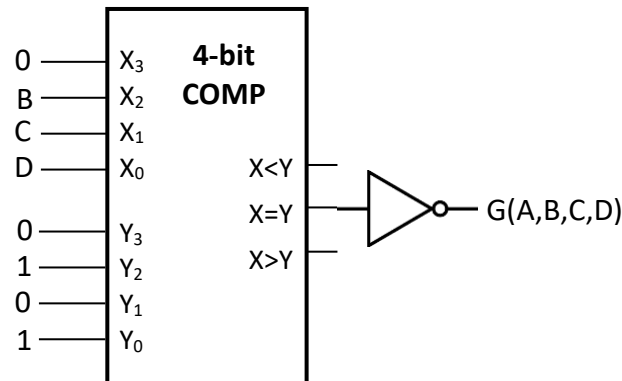

(c) (3 marks)

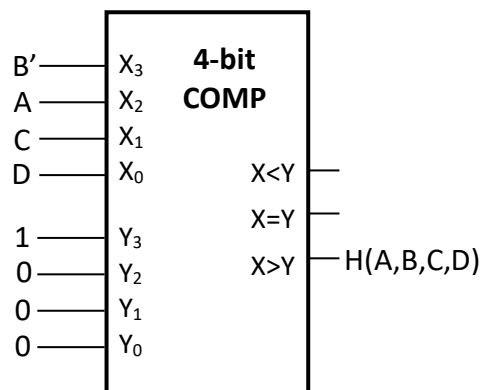

**Q4 Total: \_\_\_\_\_ / 7**

**Question 5. (5 MARKS)**

$$F_2 = A_7 + A_6 + A_5 + A_4$$

$$F_1 = A_7 + A_6 + (A_5' \cdot A_4' \cdot A_3) + (A_5' \cdot A_4' \cdot A_2)$$

$$F_0 = A_7 + (A_6' \cdot A_5) + (A_6' \cdot A_4' \cdot A_3) + (A_6' \cdot A_4' \cdot A_2' \cdot A_1)$$

**Q5 Total: \_\_\_\_\_ / 5**

**Question 6. (6 MARKS)**

(a) (2 marks) State 7

(b) (2 marks) State 2

(c) (2 marks) States 0 and 2

**Q6 Total: \_\_\_\_\_ / 6**

**Total Marks: \_\_\_\_\_ / 40 (To be filled by TA only)**

=== END OF PAPER ===